

# 一 0 0 學 年 度 第 一 學 期 數 位 電 路 學 期 中 考 試

範圍：Ch. 6~7

上課教師：潘欣泰



日期：100/12/8

1. (20%) Find the CMOS switch model networks for the following functions:


- (1) 4-input NAND gate
- (2) 3-input NOR gate
- (3) 2-input AND gate

**Answer:**

(1), (2)

  

(3) 2-input NAND + NOT

 


2. (20%) A sequential circuit is shown in Fig. 1. The timing parameters for the gates and flip-flops are as follows.

Inverter:  $t_{pd} = 0.02 \text{ ns}$

XOR gate:  $t_{pd} = 0.15 \text{ ns}$

Flip-flop:  $t_{pd} = 0.7 \text{ ns}$ ,  $t_s = 0.2 \text{ ns}$ , and  $t_h = 0.1 \text{ ns}$

 - (1) Find the longest path delay from an external circuit input passing through gates only to an external circuit output.
- (2) Find the longest path delay in the circuit from an external input to positive clock edge.
- (3) Find the longest path delay from positive clock edge to output.
- (4) Find the longest path delay from positive clock edge to positive clock edge.



# 一 0 0 學年度第一學期 數位電路學 期中考試

範圍：Ch. 6~7

上課教師：潘欣泰

日期：100/12/8

Fig. 1

**Answer:**

(1)  $2 \times 0.15$  (delay of XOR) = 0.3 ns

(2)  $t_{pd}XOR + t_{pd}INV + t_{sFF} = 0.15 + 0.02 + 0.2 = 0.37ns$

(3)  $t_{pd}FF + 2t_{pd}XOR = 0.7 + 2 \times 0.15 = 1 ns$

(4)  $t_{pd}FF + t_{pd}XOR + t_{pd}INV + t_{sFF} = 0.7 + 0.15 + 0.02 + 0.2 = 1.07ns$

3. (20%) Given the 16-bit operand 00111010 00110110, what operation must be performed and what operand must be used

(1) to clear all odd bit positions to 0? (Assume bit positions are 15 through 0 from left to right)

(2) to set leftmost 5 bits to 1?

(3) to complement the most significant 8 bits?

**Answer:**

(1) AND with 0101 0101 0101 0101

(2) OR with 1111 1000 0000 0000

(3) XOR with 1111 1111 0000 0000

4. (20%) Use D-type flip-flops and gates to design a counter with the following repeated binary sequence: 0, 1, 4, 7.

**Answer:**

present state			next state		
A	B	C	Da	Db	Dc
0	0	0	0	0	1
0	0	1	1	0	0
0	1	0	x	x	x
0	1	1	x	x	x
1	0	0	1	1	1
1	0	1	x	x	x
1	1	0	x	x	x
1	1	1	0	0	0

$Da = AB' + B' C$  (or  $AB' + AC$ )

$Db = AB'$  (or  $AC'$ )

$Dc = C'$

5. (20%) A register cell is to be designed for an 8-bit register R0 that has the following register transfer functions:

# 一 0 0 學年度第一學期 數位電路學 期中考試

範圍：Ch. 6~7

上課教師：潘欣泰

日期：100/12/8

$$\overline{S1} \cdot \overline{S0} : R0 \leftarrow R0 \oplus R1$$

$$\overline{S1} \cdot S0 : R0 \leftarrow R0 \vee R1$$


$$S1 \cdot \overline{S0} : R0 \leftarrow \overline{R0} \oplus R1$$

$$S1 \cdot S0 : R0 \leftarrow R0 \wedge R1$$

Find optimum logic using AND, OR, and NOT gates for the *D* input to the *D* flip-flop in the cell.

**Answer:**

設計過程可以斟酌給分

 

6. (20%) Design a counter that has a repeated sequence of six states as listed in following table.

Present State			Next State		
A	B	C	DA = DB = DC = A(t+1)B(t+1)C(t+1)		
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	0	0	0

**Answer:**

$$D_A = A \oplus B$$

$$D_B = C$$

$$D_C = \overline{BC}$$

一〇〇學年度第一學期 數位電路學 期中考試

範圍：Ch. 6~7

上課教師：潘欣泰

日期：100/12/8

