

CSA051 - Digital Systems

數位系統導論

# Chapter 6

## Registers and Counters

吳俊興

國立高雄大學 資訊工程學系

# Chapter 6 Registers and Counters

6-1 Registers

6-2 Shift Registers


6-3 Ripple Counters

6-4 Synchronous Counters

6-5 Other Counters

6-6 HDL for Registers and Counters


# 6-1 Registers

 


- Clocked sequential circuit
  - No flip-flops / no feedbacks → reduce to combinational circuit
  - No combinational circuit → remain a sequential circuit
    - registers and counters
- Register: a group of flip-flops capable of storing one bit of information
  - n-bit register consists of a group of n flip-flops capable of storing n bits
- Counter: a register going through a predetermined sequence of states
 
# 4-bit Register

- Simplest register: consisting of only flip-flops without any gates
- Example 6-1: 4-bit register
  - positive edge trigger
  - When the clear input goes to 0, all flip-flops are reset
  - The R inputs must be maintained at logic 1 during normal clocked operation



(a) Circuit diagram

 

(b) Graphic symbol

$R$	$C$	$D$	$Q$	$Q'$
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0

(c) Function table

Fig. 5-14 D Flip-Flop with Asynchronous Reset

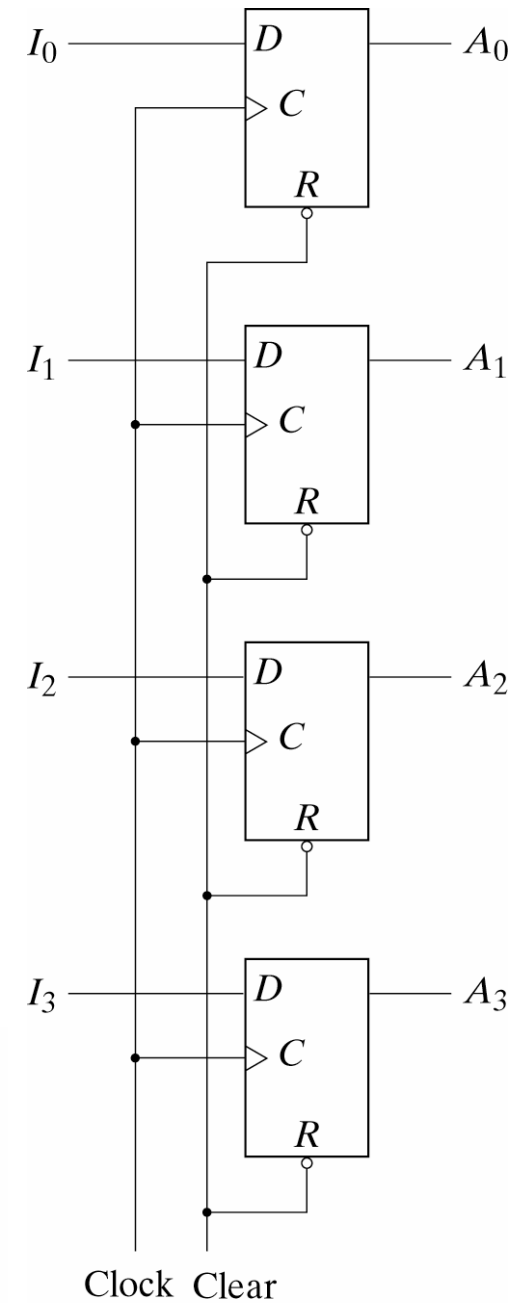


Fig. 6-1 4-Bit Register

# Register with Parallel Load


## Parallel load

- loading: the transfer of new information into a register
- parallel loading: all the bits of the register are loaded simultaneously with a common clock pulse
  - **Load control**: determine when to load new information

## Approaches to register with parallel load

1. controlling the clock input signal with an enabling gate:  
uneven propagation delays between the master clock and the inputs of flip-flops
2. controlling the D inputs: ensure that all clock pulses arrive at the same time anywhere in the system
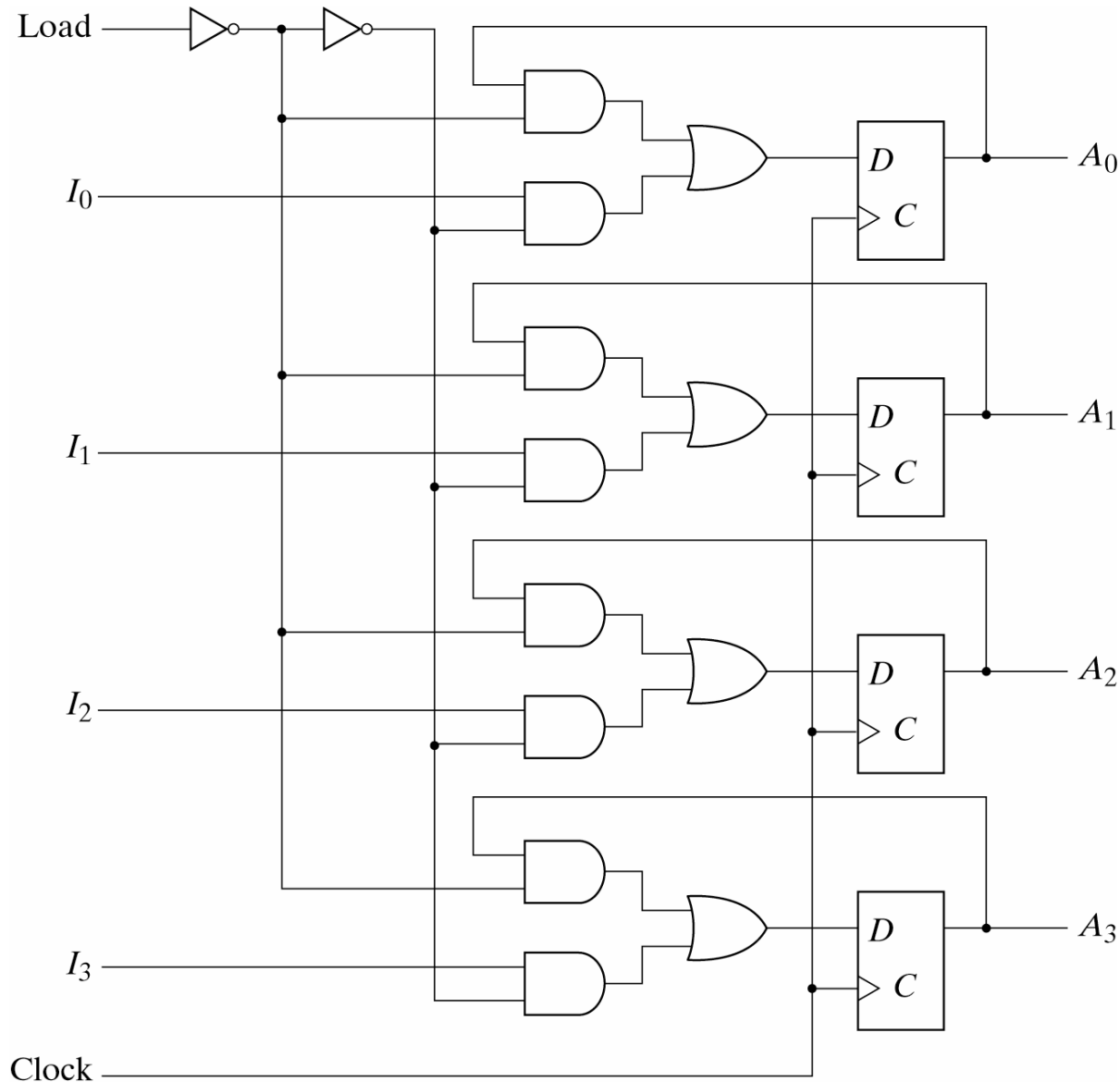
# 4-bit register with a load control input



load=1

- data are transferred into the register with the next positive edge of the clock

load=0

- outputs are connected to their respective inputs

- The feedback connection is necessary because the D flip-flop does not have a “no change” condition
- The clock pulses are applied to the C inputs at all times

Fig. 6-2 4-Bit Register with Parallel Load

## 6-2 Shift Registers

- shift register: a register capable of shifting its binary information in one or both directions
- Example Fig. 6-3: each clock pulse shifts the contents of the register one bit position to the right
  - serial input: determines what goes into the leftmost flip-flop
  - serial output: taken from the output of the rightmost flip-flop
- **Shift control:** make the shift occur only with certain pulses
  - inhibiting the clock
  - control through the D inputs (shown later)

 


Fig. 6-3 4-Bit Shift Register

# Serial Transfer

serial transfer: information is transferred one bit at a time by shifting the bits out of source register into destination register

- The serial output (SO) of register A is connected to the serial input (SI) of register B and the SI of register A itself
- The shift control input determines when and how many times the registers are shifted
- serial vs. parallel


 


Fig. 6-4 Serial Transfer from Register A to register B

**Table 6-1**  
*Serial-Transfer Example*

Timing Pulse	Register A	Register B
Initial value	1 0 1 1	0 0 1 0
After $T_1$	1 1 0 1	1 0 0 1
After $T_2$	1 1 1 0	1 1 0 0
After $T_3$	0 1 1 1	0 1 1 0
After $T_4$	1 0 1 1	1 0 1 1

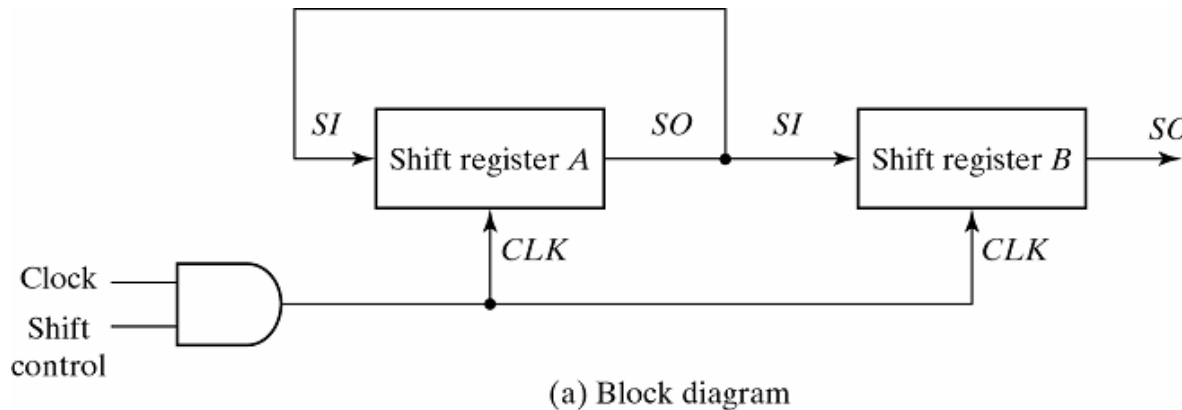


# Serial Addition

Register A holds the augend and register B holds the addend

- Initially, register A and carry flip-flop are cleared to 0

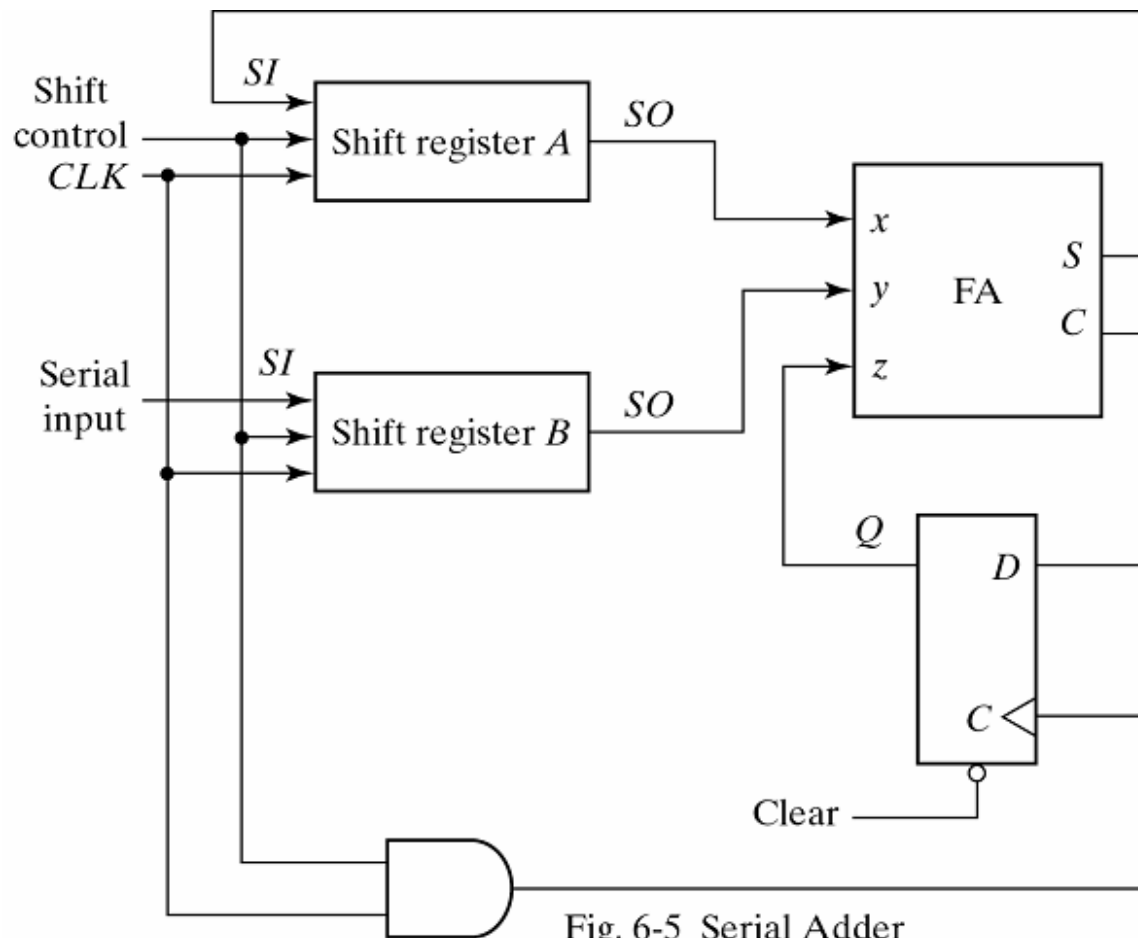All the numbers are transferred serially into B and added to A



- parallel adder: use registers with parallel load
  - # of full adders = # of bits
  - faster
  - combinational circuit
- serial adder: use shift registers
  - requiring less equipment
  - only one full adder
  - sequential circuit

# Second Form of Serial Adder

Table 6-2 State Table for Serial Adder

Present State	Inputs		Next State	Output	Flip-Flop Inputs	
	$X$	$y$			$J_Q$	$K_Q$
$Q$	$X$	$y$	$Q$	$S$	$J_Q$	$K_Q$
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0

Design a serial adder using a JK FF

- Assume 2 shift registers as input
- Obtain state table with FF input/outputs
- Obtain input and output equations
- Draw the circuit

$Q(t)$	$Q(t + 1)$	$J$	$K$
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

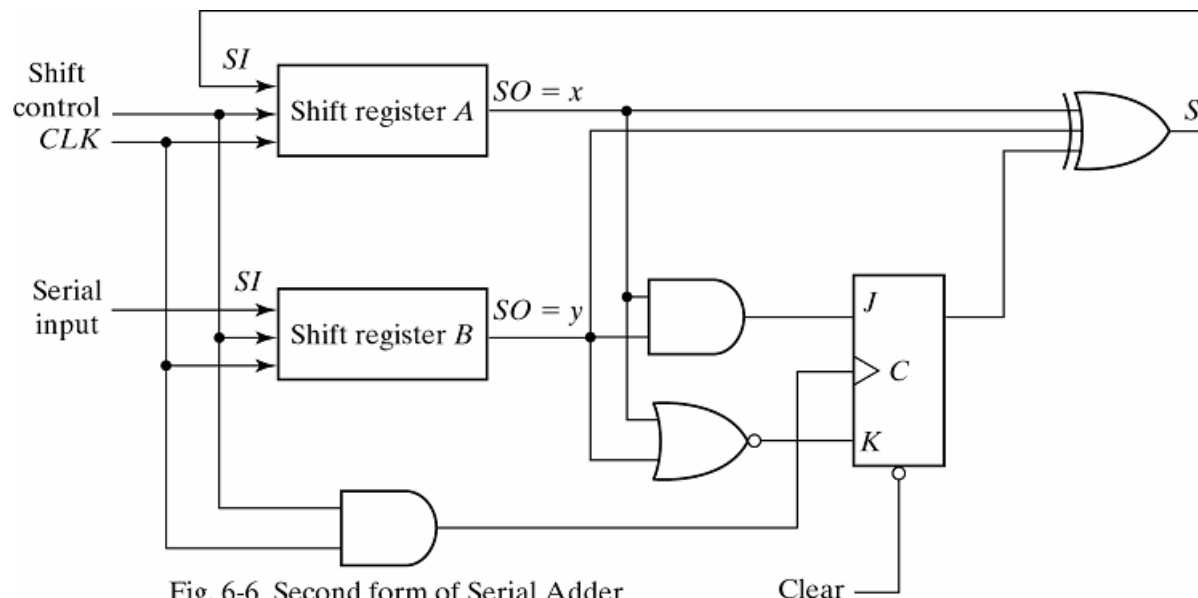


Fig. 6-6 Second form of Serial Adder

$$J_Q = xy$$

$$K_Q = x'y' = (x + y)'$$

$$S = x \oplus y \oplus Q$$

no full-adder

# Universal Shift Register

- Unidirectional shift register: capable of shifting in one direction only
- Bidirectional shift register: capable of shifting in both directions
- universal shift register: has both shifts and parallel load capabilities
- The most general shift register has the following capabilities:

1. A *clear* control to clear the register to 0.
2. A *clock* input to synchronize the operations.
3. A *shift-right* control to enable the shift right operation and the *serial input* and *output* lines associated with the shift right.
4. A *shift-left* control to enable the shift left operation and the *serial input* and *output* lines associated with the shift left.
5. A *parallel-load* control to enable a parallel transfer and the  $n$  input lines associated with the parallel transfer.
6.  $n$  parallel output lines.
7. A control state that leaves the information in the register unchanged in the presence of the clock.

# 4-bit Universal Shift Register

Has all the capabilities listed above

Selection inputs control the mode of operation

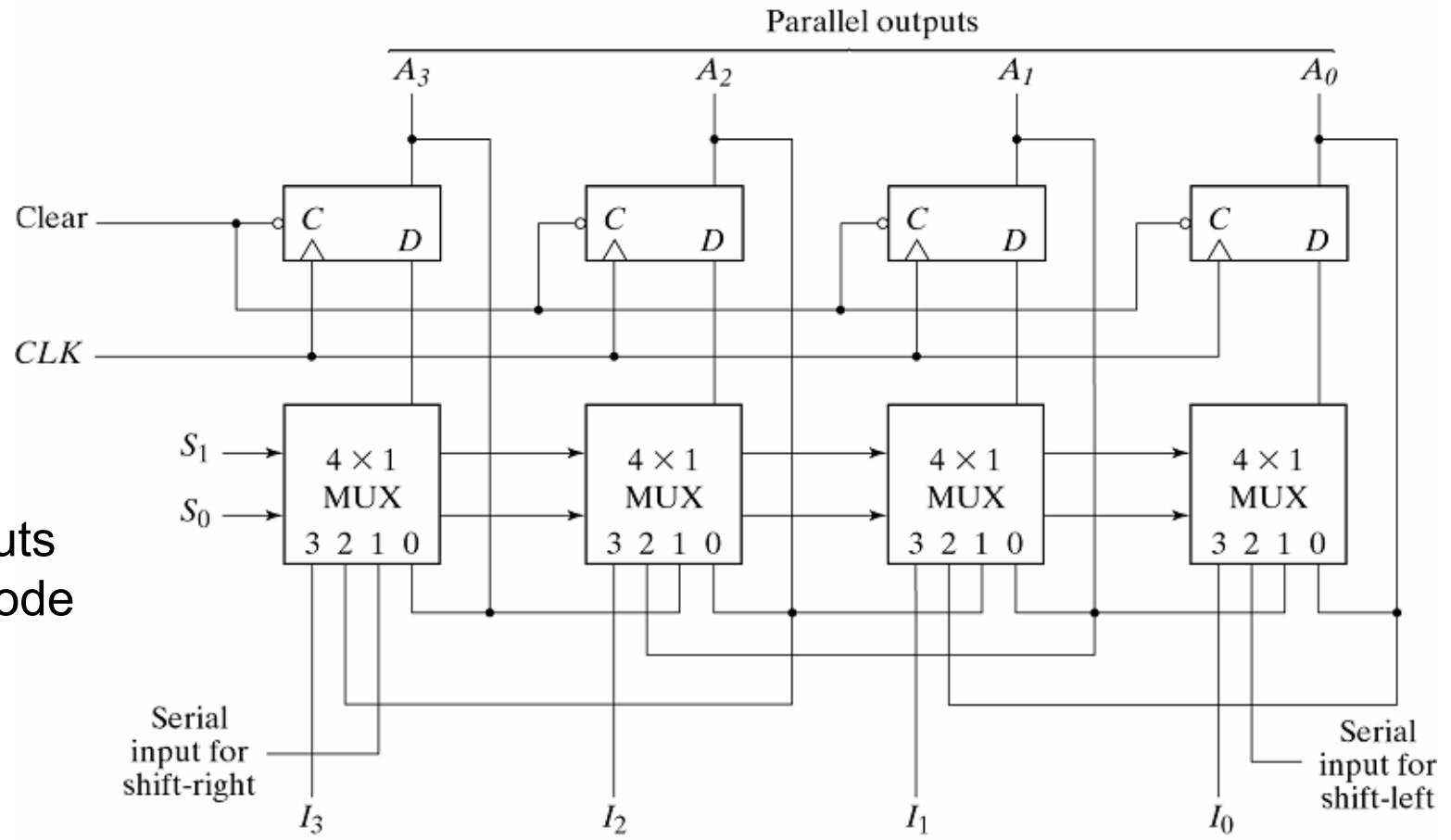


Table 6-3 Function Table for the Register of Fig. 6-7

Mode Control		Register Operation	
$s_1$	$s_0$		
0	0	No change	$A_i$
0	1	Shift right	$A_{i+1}$
1	0	Shift left	$A_{i-1}$
1	1	Parallel load	$I_i$


Parallel inputs Fig. 6-7 4-Bit Universal Shift Register

Shift registers are often used to interface digital systems situated remotely from each other

## 6-3 Ripple Counters

- **counter**: a register that goes through a prescribed sequence of states upon the application of input pulses
  - may occur at a fixed interval of time or at random
  - may follow the binary number sequence or any other sequence of states
  - n-bit **binary counter**: n flip-flops counting in binary from  $0 \sim 2^n - 1$
- Two categories
  - **Ripple counters**: FF output transition serves as a source for triggering other via the clock pin
    - Binary ripple counter
    - BCD ripple counter
  - **Synchronous counters**: inputs of all FF receive the common clock
    - discussed in Sections 6-4 and 6-5

# Figure 6-8 4-Bit Binary Ripple Counter

 

- One single count input
- Output of each FF connected to C input of next higher-order FF
- Three approaches
  - from T
  - from JK: J and K inputs tied together
  - from D: complement output connected to the D input

*Binary Count Sequence*

$A_3$	$A_2$	$A_1$	$A_0$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0

Every time  $A_i$  goes from 1 to 0, it complements  $A_{i+1}$  (Negative trigger)

$A_3$	$A_2$	$A_1$	$A_0$
1	1	1	1
1	1	1	0
1	1	0	1
1	1	0	0
1	0	1	1
1	0	1	0
1	0	0	1
1	0	0	0
0	1	1	1

- Binary count-down counter
- use positive-trigger T flip-flops instead

# BCD Ripple Counter

 


Fig. 6-9 State Diagram of a Decimal BCD-Counter

- Decade decimal counter: 0 ~ 9
- Need at least 4 flip-flops, similar to a binary counter, but state after 1001 is 0000

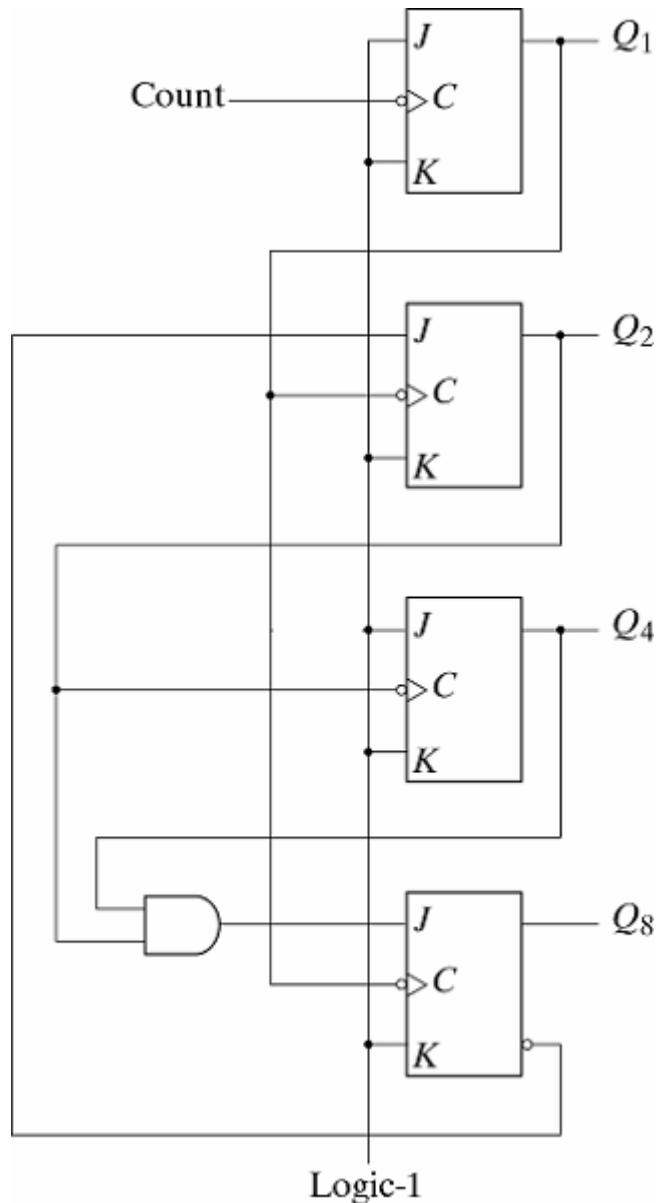


Fig. 6-10 BCD Ripple Counter

$Q_8$	$Q_4$	$Q_2$	$Q_1$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
0	0	0	0

$Q_1$ : count input

$Q_2$ :  $Q_1$  negative-edge and  $Q_8 = 0$

$Q_4$ :  $Q_2$  negative-edge

$Q_8$ :  $Q_1$  negative-edge and  $Q_2=Q_4$

$J$	$K$	$Q(t+1)$	$JK$ Flip-Flop
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

# Three-Decade Decimal BCD Counter

- n-decade counter: count from 0 to  $10^n - 1$
- Input to  $n^{\text{th}}$  decades come from  $Q_8$  of the previous  $(n-1)^{\text{th}}$  decade
- When  $Q_8$  in one decade goes from 1 to 0, it triggers the count for the next higher-order decade while its own decade goes from 9 to 0

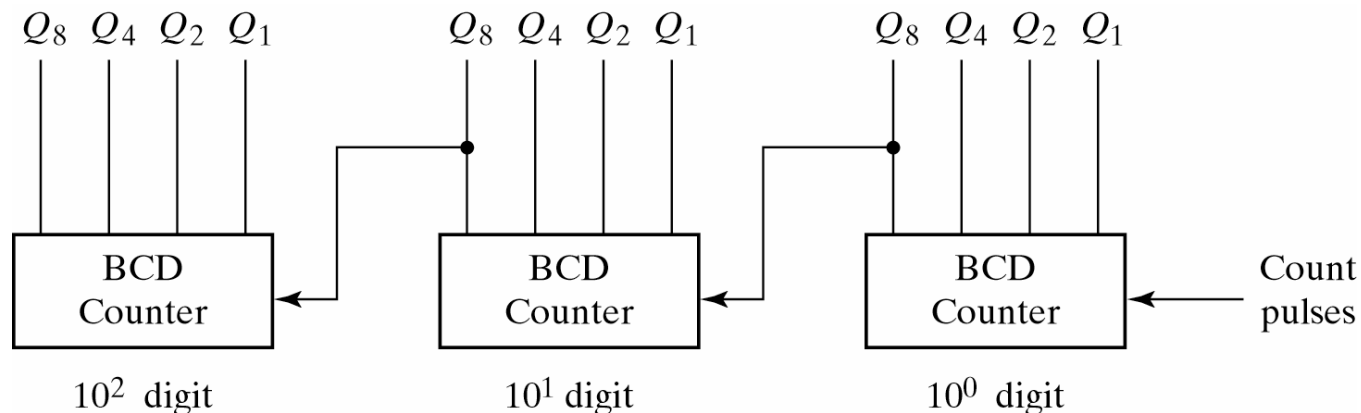


Fig. 6-11 Block Diagram of a Three-Decade Decimal BCD Counter



# 6-4 Synchronous Counters

- synchronous counter: clock pulses are applied to inputs of all FF
- 3-bit binary counter with T flip-flops

 


Fig. 5-29 State Diagram of 3-Bit Binary Counter


 


Fig. 5-31 Logic Diagram of 3-Bit Binary Counter

$$T_{A_2} = A_1 A_0 \quad T_{A_1} = A_0 \quad T_{A_0} = 1$$


# 4-Bit Synchronous Binary Counter

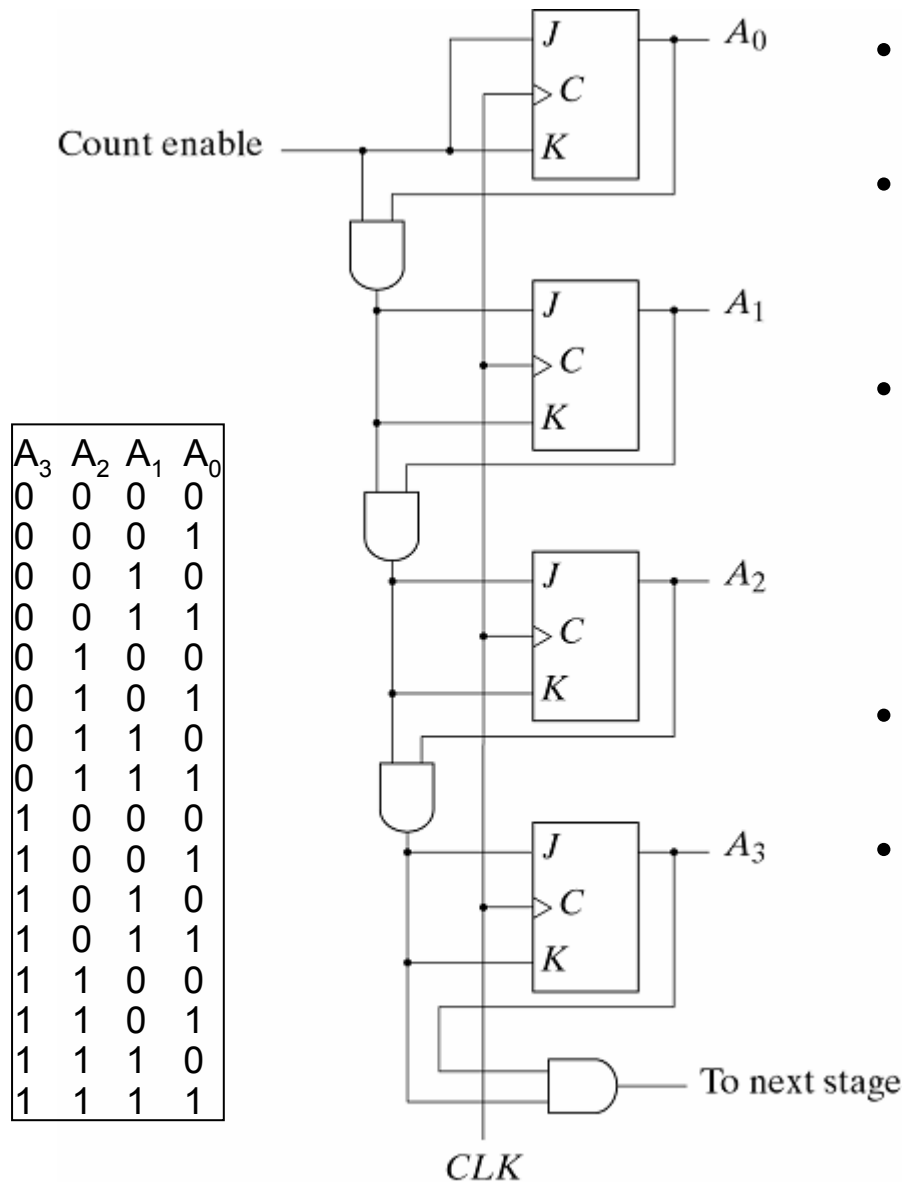

- least significant position: complemented with every pulse
- any other positions: complemented if all lower significant bits are **equal to 1**
- It can be extended to any number of stages, with each stage having an addition FF and an AND gate that gives the output of 1 if all previous FF outputs are 1
- It can be triggered with either the positive or the negative clock edge
- It can be either of the JK-type, the T-type, or the D-type with XOR gates


Fig. 6-12 4-Bit Synchronous Binary Counter

# Synchronous Count Down Binary Counter

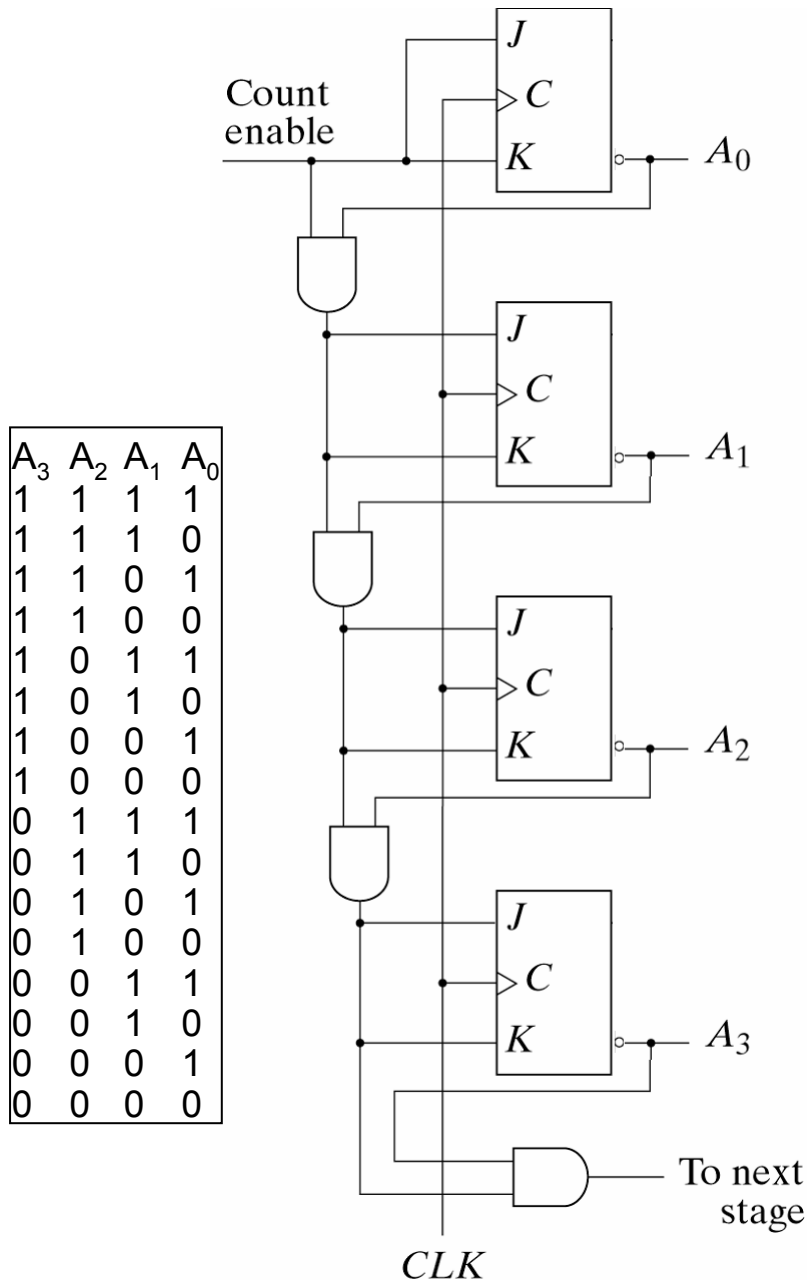

- similar to 4-Bit synchronous count up binary counter
- least significant position: complemented with every pulse
- any other positions: complemented if all lower significant bits are **equal to 0**

# Up-Down Binary Counter

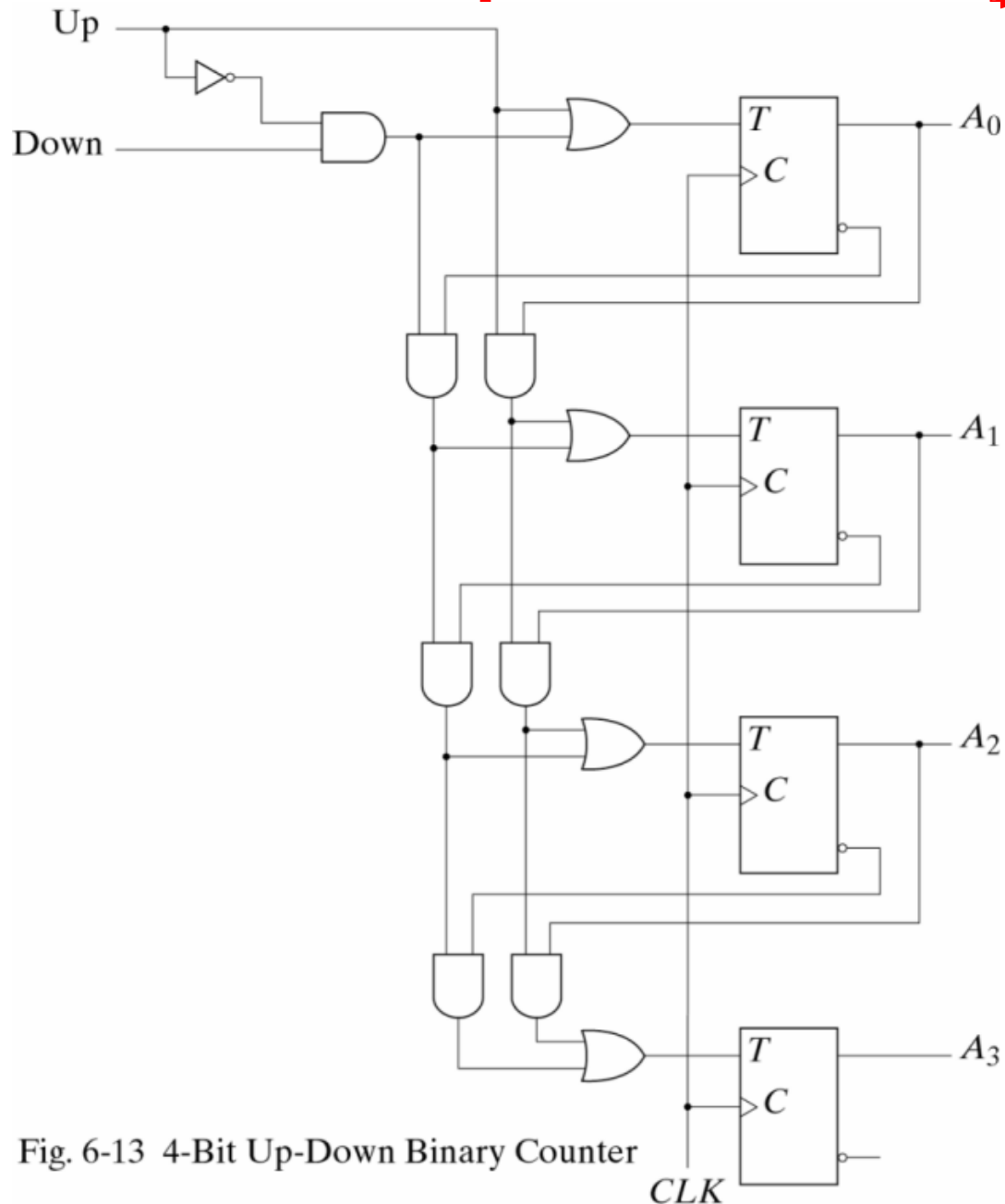

up	down	operation
1	x	count up
0	1	count down
0	0	no change

an up-down binary counter  
using T flip-flops

Fig. 6-13 4-Bit Up-Down Binary Counter

# BCD Counter

count from 0000 to 1001 and back to 0000

Table 6-5 State Table for BCD Counter

Present State				Next State				Output	Flip-Flop Inputs			
$Q_8$	$Q_4$	$Q_2$	$Q_1$	$Q_8$	$Q_4$	$Q_2$	$Q_1$	$y$	$TQ_8$	$TQ_4$	$TQ_2$	$TQ_1$
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

minterms 10 to 15 are taken as don't-care terms

$$\begin{aligned}T_{Q1} &= 1 \\T_{Q2} &= Q_8'Q_1 \\T_{Q4} &= Q_2Q_1 \\T_{Q8} &= Q_8Q_1 + Q_4Q_2Q_1 \\y &= Q_8Q_1\end{aligned}$$

4 T flip-flops, 5 AND gates, and 1 OR gate

# Binary Counter with Parallel Load

Load an initial binary number into the counter prior to the count operation

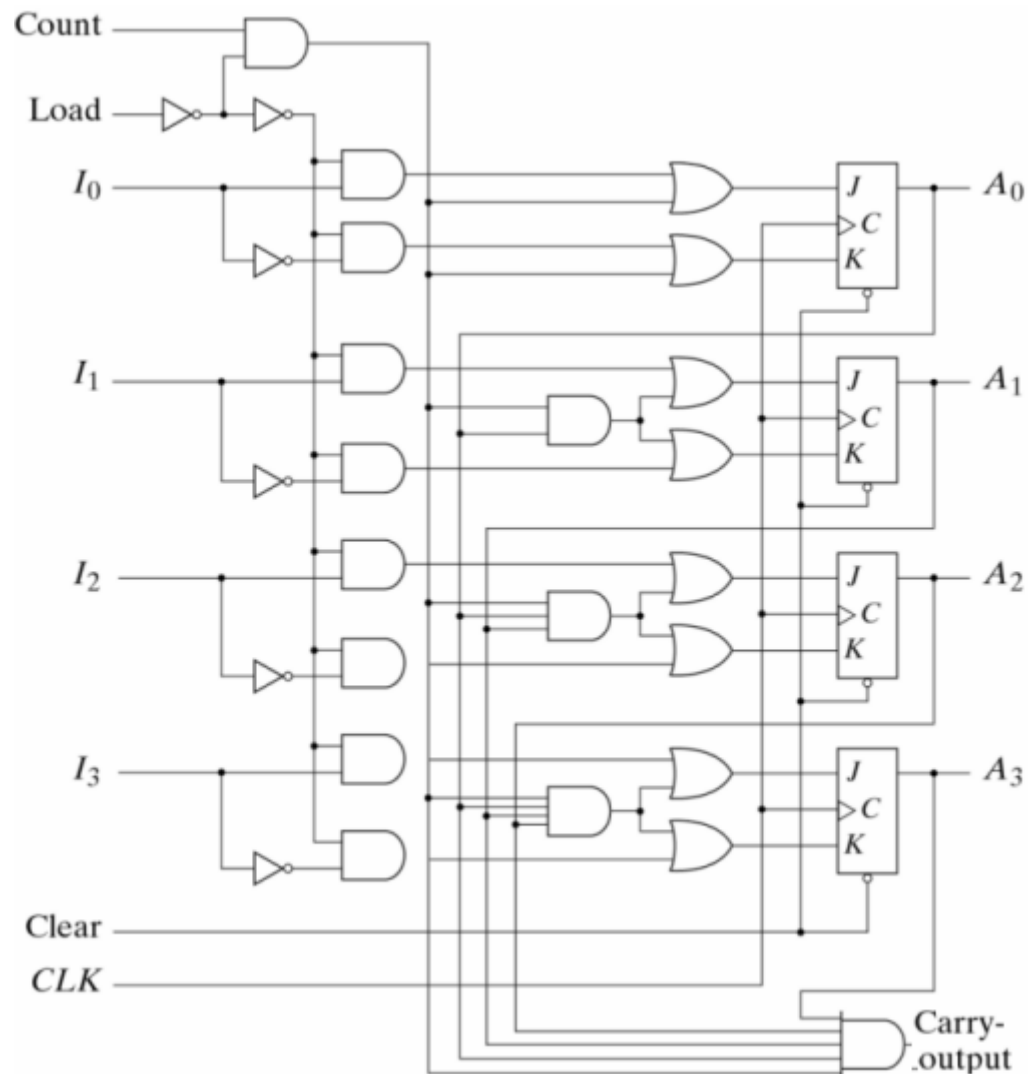


Fig. 6-14 4-Bit Binary Counter with Parallel Load

**Table 6-6 Function Table for the Counter of Fig. 6-14**

Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

**Table 5-1 Flip-Flop Characteristic Tables**

***JK* Flip-Flop**

<i>J</i>	<i>K</i>	$Q(t + 1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

It can be used to generate any desired count sequence

# A BCD Counter using a Binary Counter with Parallel Load

The AND detects the occurrence of state 1001 and then the counter reloads 0

The NAND detects the occurrence of state 1010 and then the counter is cleared to 0


 


Fig. 6-15 Two ways to Achieve a BCD Counter Using a Counter with Parallel Load
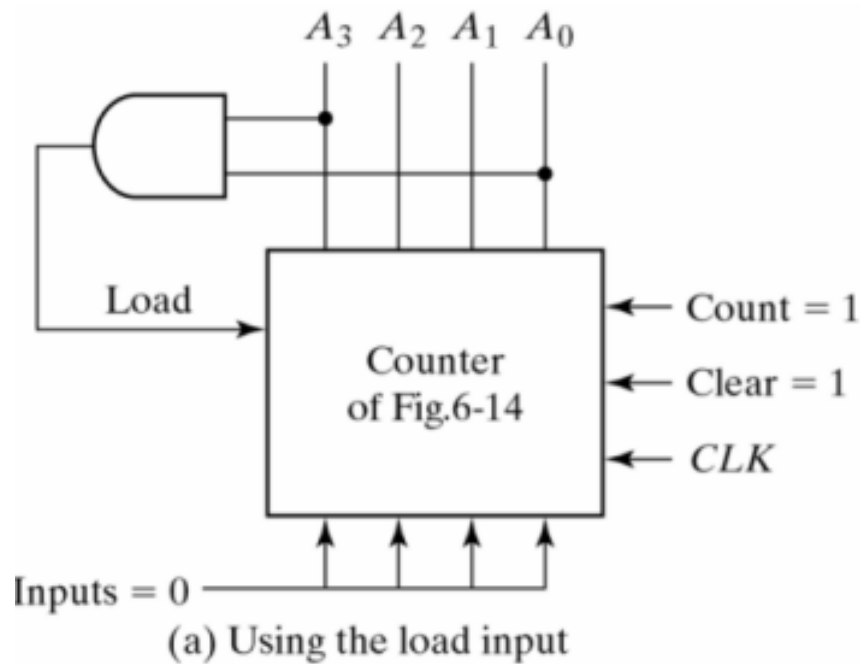
## 6-5 Other Counters

- Divide-by-N counter (modulo-N counter): a counter that goes through a repeated sequence of N states
- Counters can be used to generate timing signals to control the sequence of operations in a digital system
- Counters can be constructed also by means of shift registers
- The sequence of counters may follow the binary count or may be any other arbitrary sequence
- non-binary counters
  - Ring counter
  - Johnson counter



# Counter with Unused States

- Outside interference may cause a circuit to enter one of the unused states
- Example:

Table 6-7 State Table for Counter

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	$J_A$	$K_A$	$J_B$	$K_B$	$J_C$	$K_C$
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

two unused states: 011 and 111

Simplified equations:

$$J_A = B \quad K_A = B$$

$$J_B = C \quad K_B = 1$$

$$J_C = B' \quad K_C = 1$$

*We need to analyze the circuit to determine the effects of unused states!*


 
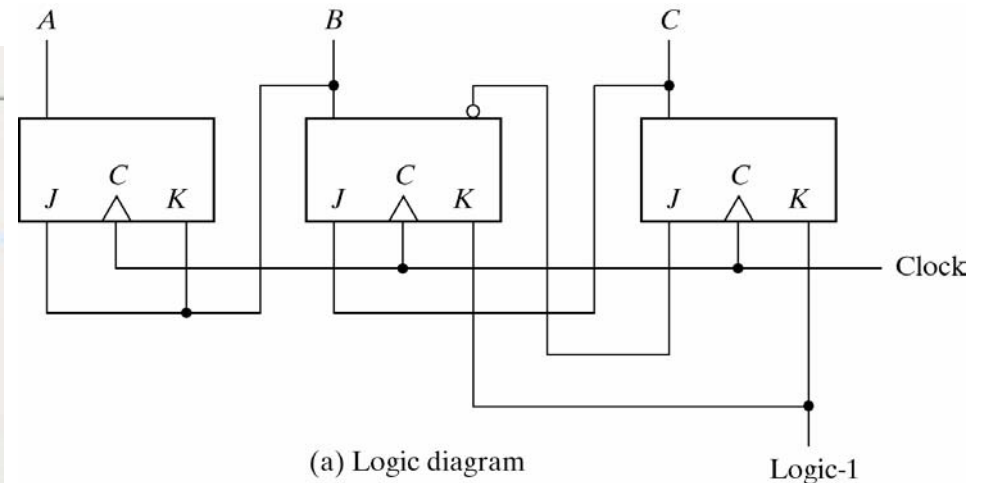


Fig. 6-16 Counter with Unused States


Self correcting counter: if it happens to be in an unused state, it eventually reaches the normal counter sequence after one or more clock pulses
 
# Ring Counter


- ring counter: a circuit shift register with only one flip-flop being set at any particular time, all others are cleared. The single bit is shifted from one flip-flop to the next to produce the sequence of timing signals
- Two approaches: (a) ring-counter (b) counter and decoder
- k-bit ring counter: k flip-flops to provide k distinguishable states



(c) Sequence of four timing signals

 

(a) Ring-counter (initial value = 1000)

 

(b) Counter and decoder


Fig. 6-17 Generation of Timing Signals

# Johnson Counter

**switch-tail ring counter:** a circular shift register with the complement output of the last flip-flop connected to the input of the first flip-flop

- double the number of states for a ring counter (Figure 6-17a)

 **Johnson counter:** a k-bit switch-tail counter with 2k decoding gates to provide outputs for 2k timing signals



Connecting Figure 6-18a with 8 AND gates listed Figure 6-18b to complete the construction of the Johnson counter

Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	$AB'$
3	1	1	0	0	$BC'$
4	1	1	1	0	$CE'$
5	1	1	1	1	$AE$
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

- Disadvantage: it never finds its way to a valid state if it is at an unused state
  - Correcting:  $D_C = (A+C)B$
- # of FF =  $\frac{1}{2}$  # of timing signals
- # of 2-input decoding gates = # of time signals

(b) Count sequence and required decoding  
Fig. 6-18 Construction of a Johnson Counter

# Summary

## Chapter 6 Registers and Counters

### 6-1 Registers

4-bit register, register with parallel load

### 6-2 Shift Registers

4-bit shift register, serial shift register, serial adder, second-form serial adder, universal shift register

### 6-3 Ripple Counters

4-bit binary ripple counter, count-down counter, BCD ripple counter, multi-decade BCD counter

### 6-4 Synchronous Counters

4-bit synchronous binary counter, count-down counter, up-down binary counter, BCD counter, binary counter with parallel load

### 6-5 Other Counters

ring counter, Johnson counter